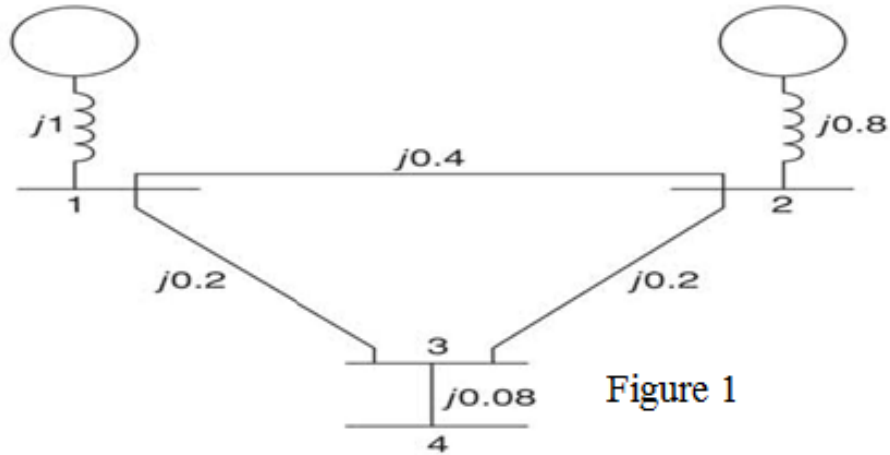
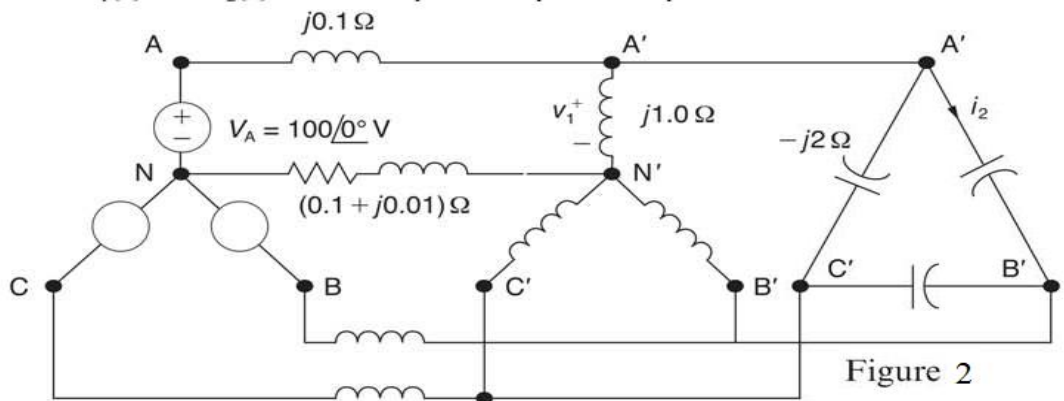


- 1- Given the impedance diagram of a simple system as shown in dal equa- Figure 1 , draw the admittance diagram for the system and develop the not solve 4×4 bus admittance matrix Y_{bus} by inspection.



- 2- Consider the balanced three-phase system shown in Figure 2 . Determine $v_1(t)$ and $i_2(t)$. Assume positive phase sequence.



- 3- Consider the balanced three-phase system shown in Figure 3 . Determine $v_1(t)$ and $i_2(t)$. Assume positive phase sequence.

